
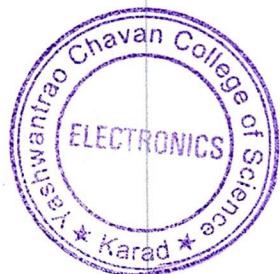


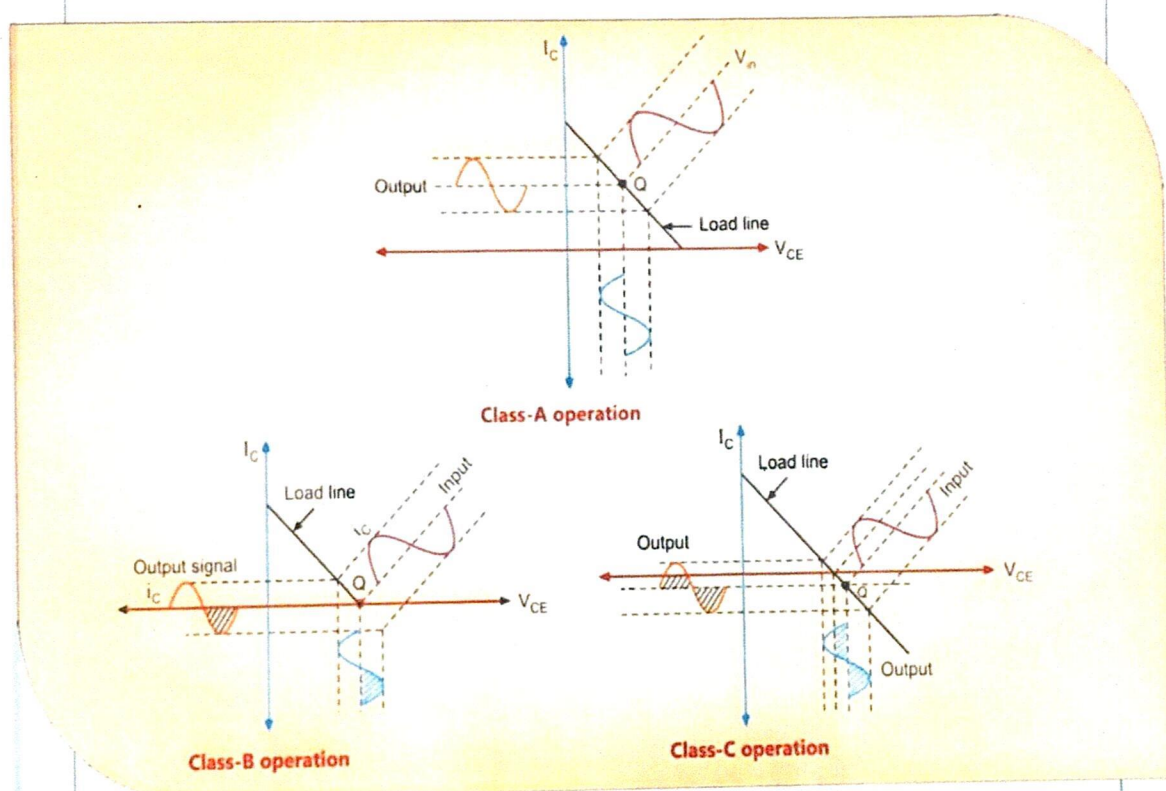As per New Syllabus (CBCS Pattern) of
Shivaji University, Kolhapur
B.Sc. Part-I : Semester-II



ANALOG ELECTRONIC CIRCUITS

(ELECTRONICS : DSC-B9 : PAPER - III)



Dr. K. D. ATAR
A. A. MULLA

Prof. (Dr.) S. R. KUMBHAR
Dr. P. U. LANDE

my
Head

Department of Electronics
Yashwantrao Chavan College Of Science, Karad

NIRALI
PRAKASHAN
ADVANCEMENT OF KNOWLEDGE

[Signature]
Principal

Yashwantrao Chavan College of Science, Karad

A TEXT BOOK OF

ELECTRONICS

ANALOG ELECTRONIC CIRCUITS

(DSC-B9 : Paper - III)

FOR

B.Sc. Part - I : Semester - II

*As Per Choice Based Credit System (CBCS) Syllabus with
Multiple Entry and Multiple Entry Options
under NEP-2020 w.e.f. June 2022 .*

Dr. K. D. ATAR

M.Sc., Ph.D., SET, NET
Assistant Professor,
Department of Electronics,
The New College, Kolhapur.

Prof. (Dr.) S. R. KUMBHAR

M.Sc., M.Phil, Ph.D., MBA, NET
Vice Principal,
Willingdon College, Sangli.

A. A. MULLA

M.Sc., SET
Assistant Professor,
Department of Electronics,
Yashwantrao Chavan
College of Science, Karad.


Dr. P. U. LANDE

M.Sc., Ph.D., SET
Assistant Professor and Head
Department of Electronics,
Government of Maharashtra's,
Rajaram College, Kolhapur.

Price : ₹ 60.00

 **NIRALI[®]**
PRAKASHAN
ADVANCEMENT OF KNOWLEDGE

N6719

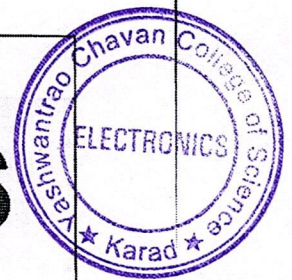

B.Sc. I : Sem. II : ELECTRONICS (P-III)

First Edition : January 2024

© : Authors

ISBN 978-93-6109-931-1



The text of this publication, or any part thereof, should not be reproduced or transmitted in any form or stored in any computer storage system or device for distribution including photocopy, recording, taping or information retrieval system or reproduced on any disc, tape, perforated media or other information storage device etc., without the written permission of Authors with whom the rights are reserved. Breach of this condition is liable for legal action.

Every effort has been made to avoid errors or omissions in this publication. In spite of this, errors may have crept in. Any mistake, error or discrepancy so noted and shall be brought to our notice shall be taken care of in the next edition. It is notified that neither the publisher nor the authors or seller shall be responsible for any damage or loss of action to any one, of any kind, in any manner, therefrom. The reader must cross check all the facts and contents with original Government notification or publications.

Published By :

NIRALI PRAKASHAN

Abhyudaya Pragati, 1312, Shivaji Nagar,

Off J.M. Road, Pune - 411005

Tel - (020) 25512336/37/39

Email : niralipune@pragationline.com

Polyplate

Printed By : YOGIRAJ PRINTERS AND BINDERS

Survey No. 10\1A, Ghule Industrial Estate,

Nanded Gaon Road,

Nanded, Pune - 411041

DISTRIBUTION CENTRES

PUNE

Nirali Prakashan

(For orders outside Pune)

S. No. 28/27, Dhayari Narhe Road, Near Asian College

Pune 411041, Maharashtra

Tel : (020) 24690204; Mobile : 9890997937

Email : bookorder@pragationline.com

Nirali Prakashan

(For orders within Pune)

119, Budhwar Peth, Jogeshwari Mandir Lane
Pune 411002, Maharashtra

Mobile : 9657703145, 9890997937

Email : niralilocal@pragationline.com

MUMBAI

Nirali Prakashan

Rasdhara Co-op. Hsg. Society Ltd., 'D' Wing Ground Floor, 385 S.V.P. Road
Girgaum, Mumbai 400004, Maharashtra

Mobile : 7045821020, Tel : (022) 2385 6339 / 2386 9976

Email : niralimumbai@pragationline.com

DISTRIBUTION BRANCHES

DELHI

Nirali Prakashan

Room No. 2 Ground Floor
4575/15 Omkar Tower, Agarwal
Road Darya Ganj, New Delhi
110002

Mobile :

9555778814/9818561840

Email : delhi@niralibooks.com

KOLHAPUR

Nirali Prakashan

438/2, Bhosale Plaza, Ground
Floor, Khasbag, Opp. Balgopal
Talim, Kolhapur 416 012

Maharashtra

Mob : 9850046155

Email :

kolhapur@niralibooks.com

BENGALURU

Nirali Prakashan

Maitri Ground Floor, Jaya
Apartments, No. 99, 6th Cross,
6th Main, Malleswaram,
Bengaluru 560003 Karnataka;

Mob : 9686821074

Email :

bengaluru@niralibooks.com

JALGAON

Nirali Prakashan

34, V. V. Golani Market, Navi
Peth, Jalgaon 425001,
Maharashtra

Tel : (0257) 222 0395

Mob : 94234 91860

Email :

jalgaon@niralibooks.com

NAGPUR

Nirali Prakashan

Above Maratha Mandir, Shop
No. 3, First Floor, Rani Jhanshi
Square, Sitabuldi Nagpur
440012 (MAH)

Tel : (0712) 254 7129

Email :

nagpur@niralibooks.com

SOLAPUR

Nirali Prakashan

R-158/2, Avanti Nagar, Near
Golden Gate, Pune Naka Chowk
Solapur 413001, Maharashtra


Mobile 9890918687

Email : solapur@niralibooks.com

marketing@pragationline.com | www.niralibooks.com


Also find us on f. www.facebook.com/niralibooks

CONTENTS

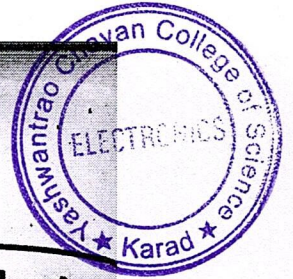

1. BIPOLAR JUNCTION TRANSISTOR	1.1 – 1.18
1.1 Introduction	1.1
1.2 Construction of a Transistor	1.1
1.3 Working of NPN Transistor	1.2
1.4 Working of PNP Transistor	1.3
1.5 Transistor Configurations	1.4
1.6 Characteristics of a Transistor	1.5
1.6.1 Characteristics of Transistor in Common Base (CB) Configuration	1.6
1.6.2 Characteristics of Transistor in Common Emitter (CE) Configuration	1.8
1.7 Transistor Regions of Operation	1.10
1.7.1 Active Region	1.10
1.7.2 Cut-Off Region	1.11
1.7.3 Saturation Region	1.11
1.8 Current Gain of Transistor	1.11
1.8.1 Current Gain of Transistor in CB Configuration	1.11
1.8.2 Current Gain of Transistor in CE Configuration	1.11
1.8.3 Relation between α and β	1.12
1.9 The Operating Point and D.C. Load Line	1.13
• Solved Problems	1.14
• Exercise	1.16
2. AMPLIFIERS	2.1 – 2.20
2.1 Introduction	2.1
2.2 Biasing of a Transistor	2.1
2.3 Need of Bias Stabilization	2.4
2.4 Fixed Biased Circuits	2.6
2.5 Voltage Divider Bias	2.8
2.5.1 Stability Factor for Potential Divider Bias	2.9
2.6 Thermal Runaway	2.10
2.7 Stability Factor	2.11
2.7.1 Stability Factor (S)	2.11
2.7.2 Stability Factor (S')	2.12
2.7.3 Stability Factor (S'')	2.12
2.8 Transistor as a Two Port Network	2.12

2.9	DC Analysis of CE Amplifier	2.15
2.10	Types of Amplifiers	2.16
2.10.1	Class-A Amplifier	2.16
2.10.2	Class-B Amplifier	2.17
2.10.3	Class-C Amplifier	2.18
•	Exercise	2.19
3.	CASCADED AMPLIFIERS	3.1 – 3.7
	Introduction	3.1
3.1	Coupling Methods	3.1
3.1.1	Resistance - Capacitance (RC) Coupling	3.2
3.1.2	Transformer Coupling (TC)	3.2
3.1.3	Direct Coupling (DC)	3.3
3.2	Resistance - Capacitance Coupled Amplifier	3.3
•	Exercise	3.6
4.	FEEDBACK IN AMPLIFIERS	4.1 – 4.14
4.1	Concept of Feedback	4.1
4.2	Theory (General Characteristics) of Feedback Circuits	4.2
4.3	Negative Feedback	4.3
4.4	Positive Feedback	4.4
4.5	Advantages of Negative Feedback	4.4
4.5.1	Increased Stability (Stabilisation of Gain)	4.4
4.5.2	Increased Bandwidth	4.5
4.5.3	Decreased Distortion	4.6
4.5.4	Decreased Noise	4.7
4.5.5	Input Impedance	4.7
4.5.6	Output Impedance	4.9
•	Solved Problems	4.9
•	Problems for Practice	4.12
•	Exercise	4.12
5.	SINUSOIDAL OSCILLATORS	5.1 – 5.17
5.1	Introduction	5.1
5.2	Barkhausen Criterion for Sustained Oscillations	5.2
5.3	Phase-Shift Oscillator	5.3
5.3.1	Determination of Frequency and Condition of Oscillation	5.4
5.4	Colpitt's Oscillator	5.5
5.4.1	Determination of Frequency and Condition of Oscillation	5.6
5.5	Crystal Oscillator	5.8
5.5.1	Crystal Controlled Oscillator (Miller Crystal Oscillator)	5.8

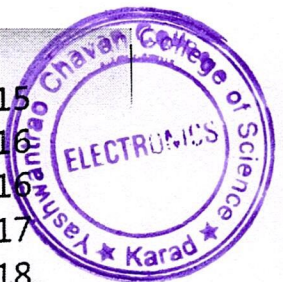

5.5.2 Pierce Crystal Oscillator

- Solved Problems
- Problems for Practice
- Exercise

6. UNIPOLAR DEVICES

6.1 Introduction

6.2 Junction Field Effect Transistor

6.2.1 Construction of JFET

6.2.2 Operation of N-Channel JFET

6.2.3 I-V Characteristics of JFET

6.2.4 JFET Parameters

6.2.5 Relation between μ , g_m and r_d

6.3 Uni-junction Transistor

6.3.1 Basic Construction of UJT

6.3.2 Operation of UJT

6.3.3 Equivalent Circuit of UJT

6.3.4 I-V Characteristics of a UJT

- Exercise

**NATURE OF QUESTION PAPER FOR CBCS PATTERN
ALL UG/PG SCIENCE SUBJECTS (w.e.f. June 2022)**

Time : 2 Hrs.

Q. 1 Multiple Choice Questions :

Marks : 4

- (i) (a) (b) (c) (d)
- (ii) Do
- (iii) Do
- (iv) Do
- (v) Do
- (vi) Do
- (vii) Do
- (viii) Do

Q. 2 Attempt any Two of the following :

- (A)
(B)
(C)

Q. 3 Attempt any Four of the following :

- (a)
(b)
(c)
(d)
(e)
(f)

